

NETWORK THEOREMS -1

The loop current and node voltage methods are employed to solve all network problems. It is possible to determine all the branch currents and voltages. Sometimes, we may be interested in determine a particular branch current or voltage only. In such cases, network theorems are useful and which simplify the method of solution.




Thevenin's Theorem:

This theorem helps in reducing the given network to simple equivalent network with respect to a given pair of terminals. If a network is to be solved for the current through different load of impedances to be connected across two specified points in the network, we can employ either loop current or nodal method, but the network is to be solved as much number of times as there are different load of impedances. In such cases, it will be convenient to reduce the network to an equivalent network with respect to load terminals by applying thevenin's theorem and calculate the current for each load of impedance.

Statement:

The current in any load impedance connected to two terminals of a linear active network is the same as if this load impedance was connected to an equivalent consisting of a constant voltage source whose voltage is equal to the open circuit voltage at two terminals and whose internal impedance the impedance of the network looking back into the terminals with all source within the active network replaced by impedance equal to their internal impedances.

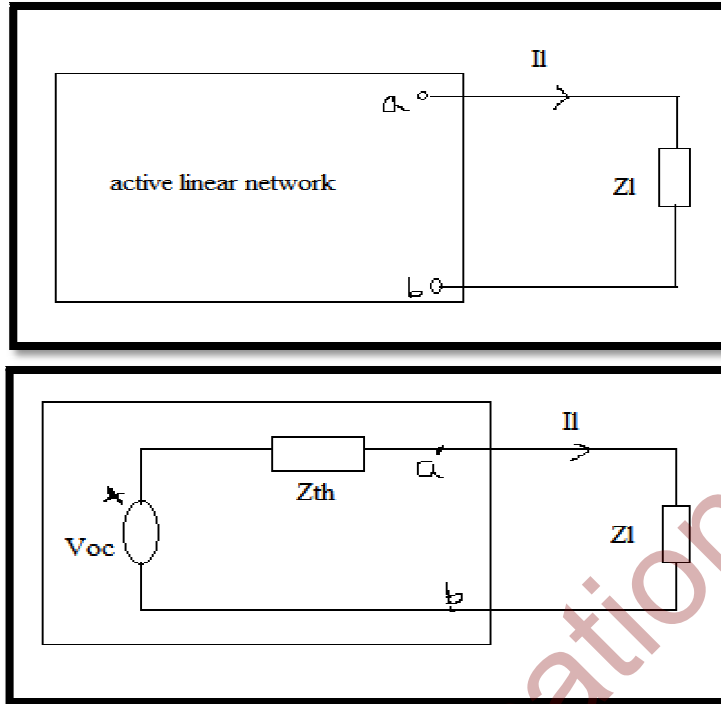

The fig shows an active linear network with two terminals a and b to which a load impedance Z_l is connected. Thevenin's theorem says that so far as its external behavior is concerned, the network can be replaced by an equivalent consisting of a voltage source V_{oc} in series with an impedance Z_{th} as indicated in fig, such that the load current remains the same in the original and equivalent circuit


$$I_l = V_{oc} / (Z_{th} + Z_l)$$

Where V_{oc} is open circuit voltage between the terminals a and b

And Z_{th} is thevenin's impedance and it is measured across the terminals a and b.

Proof: the proof makes use of superposition theorem

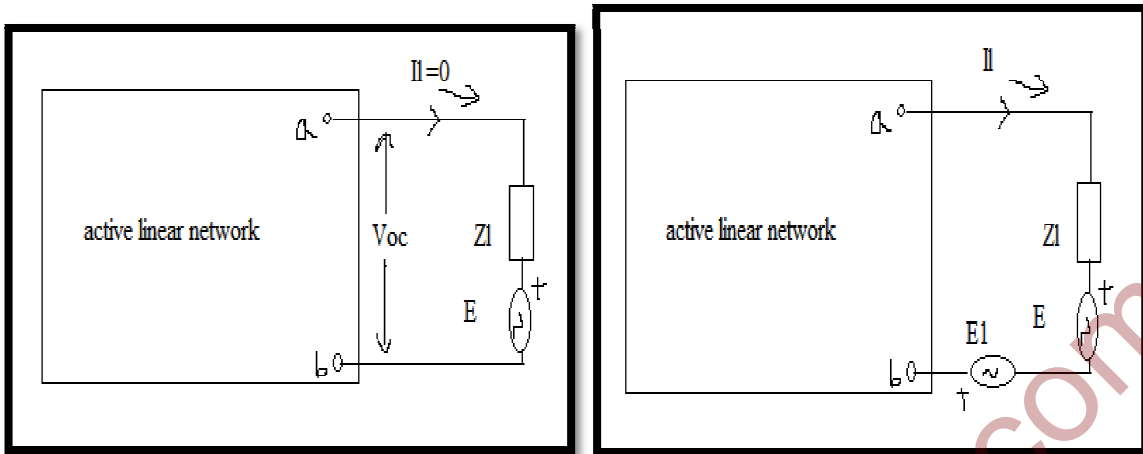step1: Let us suppose that in the load circuit of fig is introduced a voltage source E of such a magnitude and direction that the load current reduced to zero.



Evidently the magnitude of the source E should be equal to the open circuit voltage, V_{oc} of the active network at the load terminals and its direction must be opposite to that of V_{oc} as indicated in fig.

Step2: let us suppose that yet another voltage source E_1 equal and opposite to the source E is introduced into the load circuit. The network is modified as that shown in fig. the introduction of the new source E_1 cause a current I_1 to flow in the external circuit. Since there was no current in the external circuit before introducing E_1 , it would mean that I_1 should be the current that would flow with E_1 alone acting in the network with all other sources reduced to zero.


Therefore the current $I_1 = E_1 / (Z_{th} + Z_l)$

Step3: since E and E_1 are equal and opposite, the resultant voltage across them is zero. The removal of the two sources E and E_1 together does not affect the current I_1 in the load circuit which is therefore the same as I . The network reverts to its original form as in fig.

$$I = I_1 = V_{oc} / (Z_{th} + Z_l)$$



This is the current that flows in the load impedance Z_l connected to an constant voltage source V_{oc} of internal impedance Z_{th} . The network in fig denotes the thevenin's equivalent of the original network in fig.

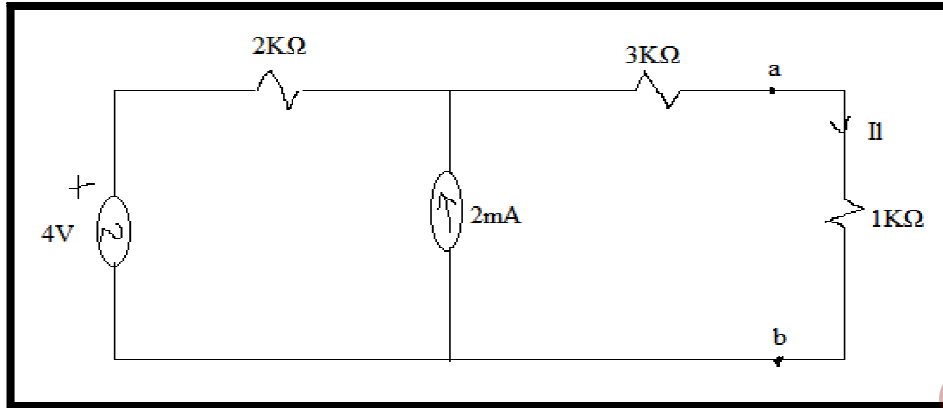Example 1: determine I using thevenin's theorem



To get thevenin's equivalent w. r. t a and b terminals

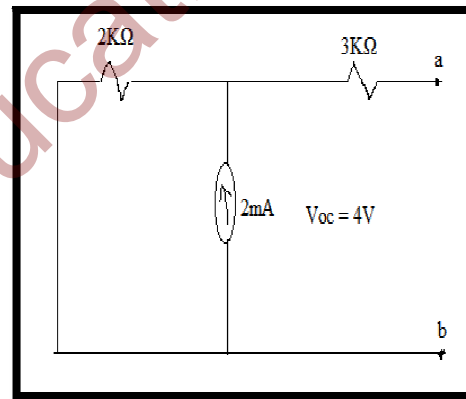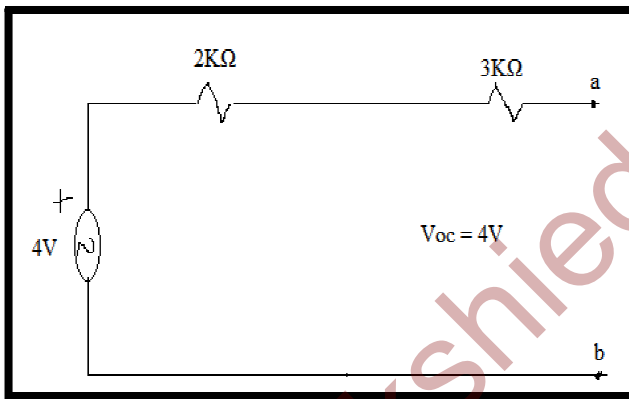
Thevenin's voltage V_{th} or V_{oc} : we will use superposition theorem to calculate V_{oc}



With 4V only, $V_{oc} = 4V$

With 2mA only, $V_{oc} = 4V$

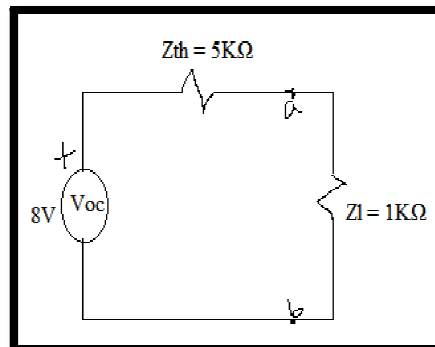From V_{oc} simultaneously acting with two sources, $V_{oc} = 8V$




Thevenin's impedance: replace all the sources by their internal impedance and determine the impedance between a and b, $Z_{th} = 5K\Omega$


From the thevenin's equivalent shown in fig,

$$I_l = V_{oc} / (Z_{th} + Z_l) = 8 / (6 * 10^3) = 4/3mA$$

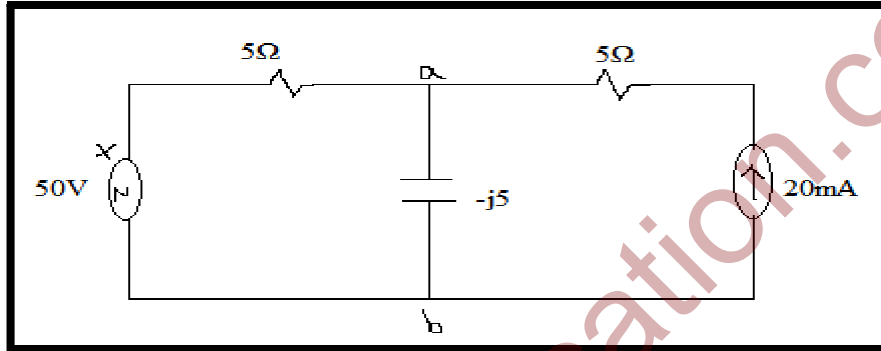
Example 2: Determine the current through the capacitor using Thevenin's theorem



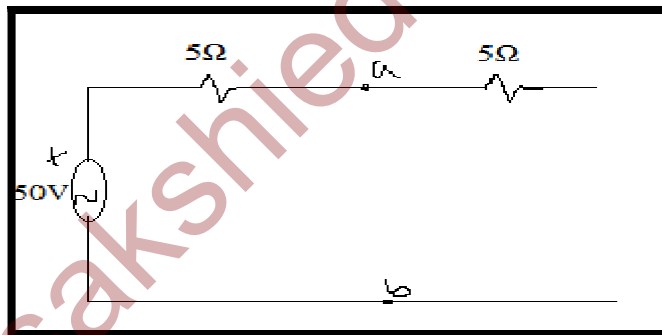Apply thevenin's theorem between terminals a and b



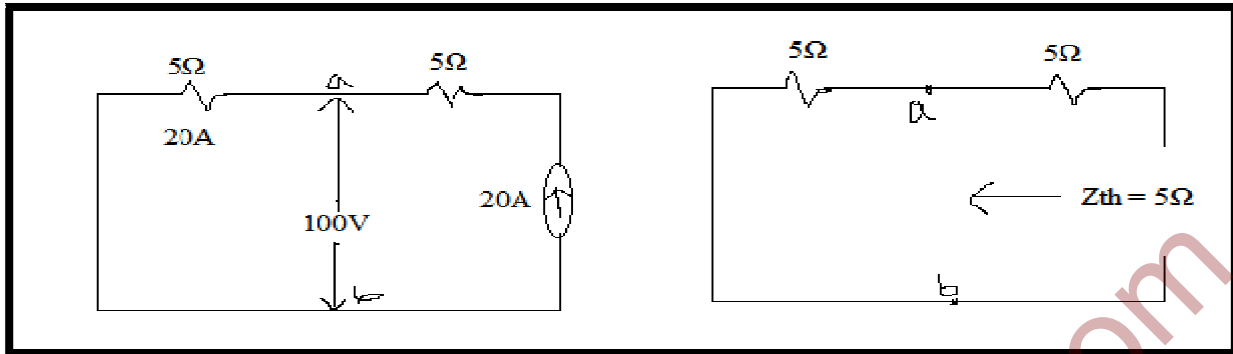Thevenin's voltage: we will employ superposition theorem to calculate V^{th} or V_{oc}



With only 50V source, $V_{oc} = 50V$


With only 20A source, $V_{oc} = 5 * 20 = 100V$

When both sources are acting simultaneously, $V_{oc} = 50 + 100 = 150V$

Thevenin's impedance:

$$Z_{th} = Z_{ab} = 5\Omega$$

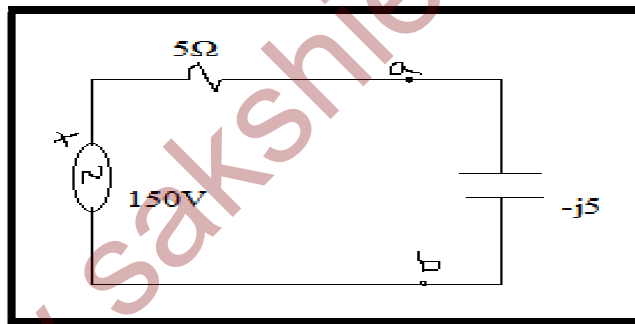The thevenin's equivalent w. r. t to a and b terminals is



Current through capacitor $I_c = V_{oc} / (Z_{th} - j5) = 150 / (5 - j5) = 15 + j15 A$

Norton's Theorem:


It is the dual of Thevenin's Theorem.

Statement:

The current in any load impedance connected to two terminals of an active linear network is the same as if this load impedance was connected to a constant current


generator whose current is equal to the current which flows through the two terminals when they are short circuited, and being in parallel with an admittance equal to the admittance of the network looking back into the terminals with all sources replaced by their internal admittances.

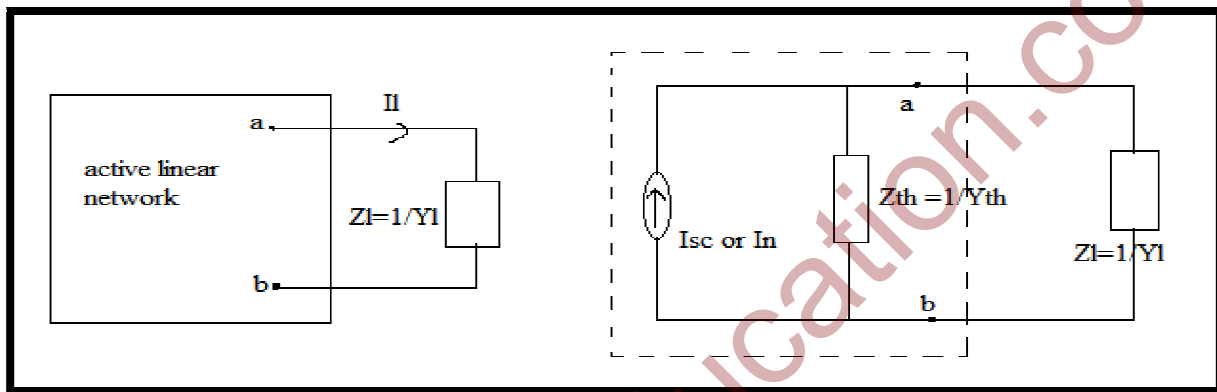The fig shows an active network which can be replaced with respect to terminals a and b by norton's theorem by an equivalent shown in fig.



The equivalent circuit consists of a current source I_{sc} in parallel with an admittance Y_{th} (Admittance looking back into the network from terminals a and b when all the sources replaced by their internal admittances).

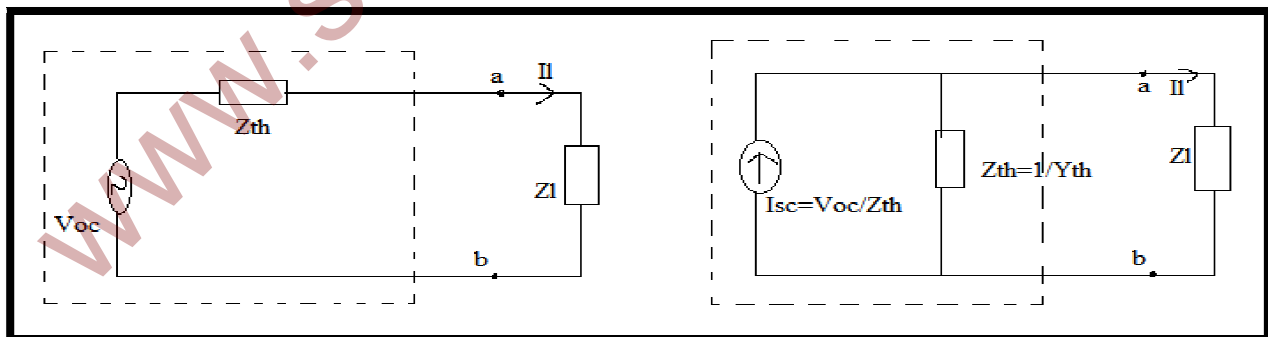Proof: The proof of the theorem follows from that of thevenin's theorem. By thevenin's theorem the active network reduced to an equivalent network consisting of a constant voltage (V_{oc} or V_{th}) and series impedance Z_{th} .



Replace the constant voltage generator V_{oc} in series with the impedance Z_{th} by an equivalent current source, $I_{sc} = V_{oc} / Z_{th}$ in shunt with impedance Z_{th} or

admittance $Y_{th} = 1 / Z_{th}$ as shown in fig. Norton's theorem is hence proved. An independent proof also be given for Norton's theorem.

By Norton's theorem $I_2 = I_{sc} * (Z_{th} / Z_{th} + Z_l)$

Where $I_{sc} = V_{oc} / Z_{th}$


Hence $I_2 = V_{oc} / Z_{th} + Z_l$

Voltage drop across the terminals = $I_2 Z_l = (Z_{th} * Z_l / (Z_{th} + Z_l))$


$V_{ab} = I_{sc} * (1 / (Y_{th} + Y_l))$

The duality between thevenin's and norton's theorem is evident from the equations for I_2 based on thevenin's theorem and the equation for V_{ab} based on norton's theorem.

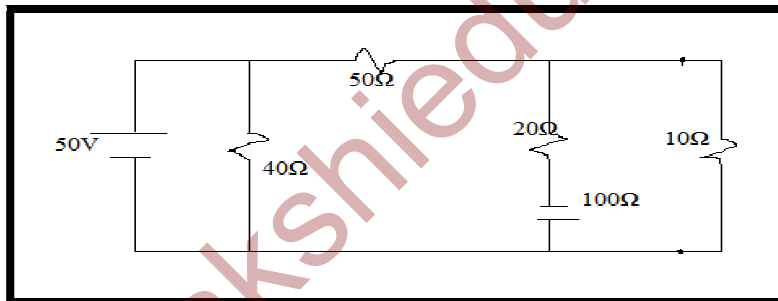Example 1: Find the voltage across the 10Ω resistance in the network shown in fig. using Norton's theorem.



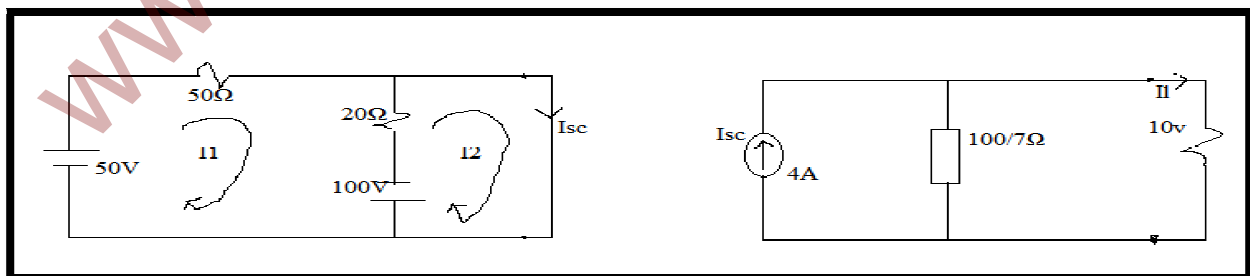A 40 Ω resistor in parallel with a 50 V source is ineffective. Short circuit 10 Ω and determine I_{sc}



Calculation of Isc:

$$50 I_1 + 20 (I_1 - I_2) = 150$$

$$70 I_1 - 20 I_2 = 150$$

$$7 I_1 - 2 I_2 = 15 \text{ ----- (1)}$$

$$20 (I_2 - I_1) = 15$$

$$I_1 - I_2 = 5 \text{ -----(2)}$$

Solve the equations (1) & (2) we get, $I_1 = 1A$ and $I_2 = -4A$


$I_{sc} = 4A$ in the up word direction.

$$R_{th} = 50 * 20 / 70 = 100/7 \Omega$$

$$\text{Current through } 10 \Omega, = (4 * 100/7) / (4 + (100/7)) = 40/17A$$

$$\text{Voltage across } 10 \Omega, = 10 * (40 / 17) = 400 / 17V$$

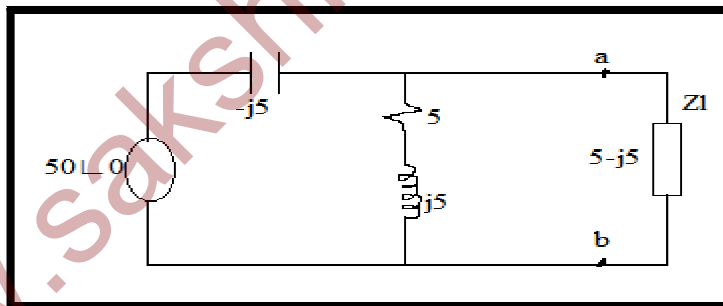
Example 2: Using the norton's theorem determine the current through load impudence $Z_L = 5-j5$ of the network shown in fig. find the power consumed by load.




Get the norton's equivalent with respect to terminals a and b

Calculation of Isc:

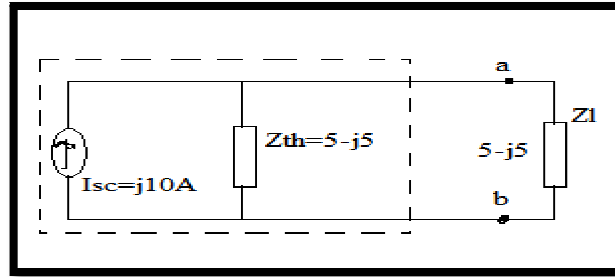
$$\text{From the circuit, } I_{sc} = 50 \angle 0 / 50 \angle -90 = 10 \angle 90 = j10A$$



Calculation of Z_{th}:

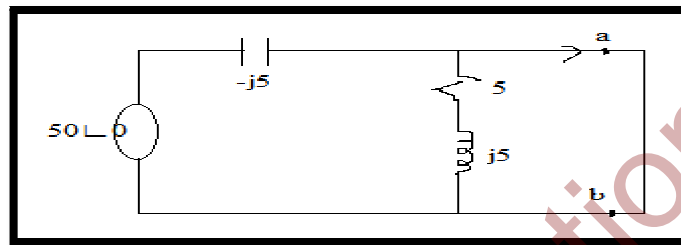

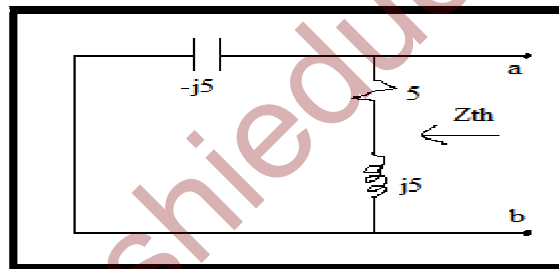From the circuit, $Z_{th} = (5 + j5)(-j5)/5 = 5 - j5$



From the Norton's equivalent, $I_l = I_{sc} * (5-j5) / (5-j5) + (5+j5) = I_{sc} / 2 = 5 \angle 90 = j5A$

Power consumed by the load, $P_l = I_l^2 * R_l = 5^2 * 5 = 125W$

Reciprocity Theorem:

Statement:

If a voltage applied in one branch of a linear, bilateral, passive network produces a certain current in any other branch of the network, the same voltage applied in the second branch will produce the same current in the first branch also.

Proof: Consider a network consists of L loops. Let the network be excited by only one voltage source E_s in the Sth loop. To determine the current response I_r in the Rth loop is given by as

$$I_r = (1/D_z)(A_{1r} E_1 + A_{2r} E_2 + \dots + A_{jr} E_j + \dots + A_{sr} E_s + A_{nr} E_n + \dots)$$

Since there is only one source in the Sth loop in the network,

$$I_r = A_{sr} * E_s / D_z = Y_{rs} . E_s$$

Let us now interchange the positions of excitation and response (exception to Rth loop and response to Sth loop). We have voltage source in the Rth loop and the response is measured in the Sth loop as I_s .

$$I_s = A_{rs} * E_r / D_z = Y_{rs} . E_r$$

The ratio of excitation to response remains constant i.e.

$$E_s / I_r = D_z / A_{sr} \quad \text{and} \quad E_r / I_s = D_z / A_{rs}$$

If they are to be equal, $A_{sr} = A_{rs}$.

For a linear bilateral network, the cofactors $A_{rs} = A_{sr}$. Since the loop impedance matrix is symmetrical.

Hence theorem is proved. Note the other parts of the network will not remain the same.

Maximum Power Transfer Theorem:


If load impedance is connected between two terminals of an active linear network, then the load impedance can be adjusted so that the power delivered to it is maximum. This process of adjusting the load impedance is known as matching the impedance to source power.

There are few theoretical aspects of matching based on the constraints placed on the parameters of the load impedance.

The general condition for maximum power transfer to the load is that the load impedance should be complex conjugate of the internal impedance of the active network.

There are 4 cases related to maximum power transfer theorem.

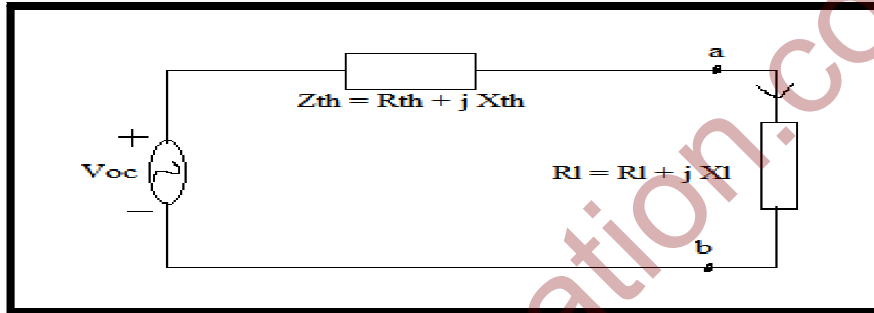Case 1: The load impedance $Z_L = R_L + jX_L$ in which both resistance and reactance can be varied, independently.



The active linear network to which the load is connected is thevenised into a single voltage source V_{oc} in series with internal impedance Z_{th} with respect to load terminals as shown in fig.

Then the power transferred to the load is $P_L = I^2 * R_L$.

Therefore $P = \frac{V_{oc}^2 R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$ (1)

Assuming first that only X_L is variable and R_L is fixed, for maximum power $\frac{dP}{dX_L} = 0$.

$$\frac{dP}{dX_L} = \frac{d}{dX_L} \left[\frac{V_{oc}^2 R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2} \right] = 0$$

Hence $X_L = -X_{th}$ (2)

Now to maximize P_L further, let R_L also be varied so that, $\frac{dP}{dR_L} = 0$

$$\frac{dP}{dR_L} = \frac{d}{dR_L} \left[\frac{V_{oc}^2 R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2} \right] = 0 \text{ (3)}$$

From equations (2) & (3) we get,

$$(R_{th} + R_l)(R_{th} - R_l) = 0 \Rightarrow R_l = R_{th} \text{ ----- (4)}$$

Therefore for the power transferred to the load is maximum, which R_l and X_l are both variable.

$$Z_l = R_{th} - j X_{th} = \text{conjugate of } Z_{th} \Rightarrow Z_l = Z_{th}^* \text{ ----- (5)}$$

The maximum power transferred to the load under this condition is

$$P_{max} = \frac{(V_{oc})^2 \cdot R_{th}}{(2R_{th})^2} = \frac{V_{oc}^2}{4 R_{th}} \text{ this is independent of } X_{th}. \text{ ----- (6)}$$

Case 2: In the load impedance Z_l only resistance is variable while reactance X_l is fixed. For maximum power the condition as given by equation (3)

$$(R_{th} + R_l)^2 + (X_{th} + X_l)^2 - 2R_l((R_{th} + R_l)) = 0$$

$$(R_{th} + R_l)(R_{th} + R_l) + (X_{th} + X_l)^2 = 0$$

$$(R_{th})^2 - (R_l)^2 + (X_{th} + X_l)^2 = 0$$

$$(R_l)^2 = (R_{th})^2 + (X_{th} + X_l)^2$$

$$R_l = \sqrt{(R_{th})^2 + (X_{th} + X_l)^2}$$

$$|R_l| = |Z_{th} + j X_l| \text{ ----- (7)}$$

Case 3: When R_l is variable and load is purely resistive i.e., $X_l = 0$. For maximum power from equation (7), $|R_l| = |Z_{th}| \text{ ----- (8)}$

i.e., the load resistance should be equal to absolute value of the thevenin's impedance of the active network.

Case 4: When the magnitude of load impedance is varied but the impedance angle of the load i.e.

$$\theta = (\tan)^{-1} \frac{X_l}{R_l} \text{ remains constant.}$$

$$\text{Let } Z_l = R_l + jX_l = Z_l (\cos\theta + j \sin\theta)$$


$$P_l = \frac{V_{oc}^2 Z_l}{(Z_l + Z_{th})^2}$$

For P_l is to be maximum Z_l only, $\frac{dP_l}{dZ_l} = 0$

From that we can solve $|Z_l| = \frac{V_{oc}^2}{2P_{max}} = |Z_{th}|$

From the above, it is seen that only when magnitude of load impedance is varied keeping impedance angle constant, max power transfer will occur when $|Z_l| = |Z_{th}|$ of the active n/w.

Milliman's Theorem:

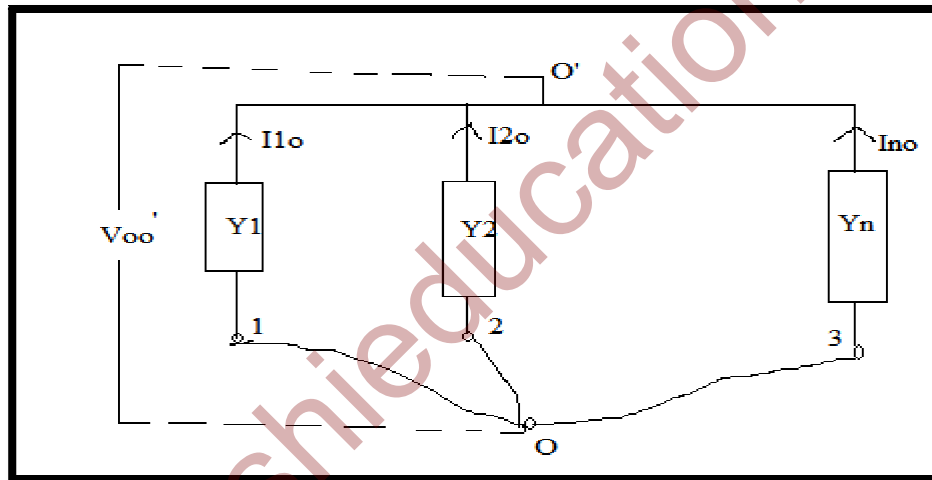

STATEMENT: This theorem states that the voltage drop from point 'O' to point 'O' junction of number of impedances in a network of the form shown in fig.

$$V_{O'O} = \frac{V_{O'O} \sum_{k=1}^n Y_k}{\sum_{k=1}^n Y_k + Y_{O'O}}$$

$$V_{O'O} = \frac{V_{O'O} Y_k}{\sum_{k=1}^n Y_k + Y_{O'O}} \text{ where } k=1 \text{ to } n$$

Where $V_{O1}, V_{O2}, \dots, V_{On}$ are the voltage drops 'O' to 1, 2, ..., n and Y_1, Y_2, \dots, Y_n are the admittance between nodes 1, 2, ..., n to common point O. In applying this theorem it is not necessary to know interconnection between O and any other point n across which voltage V_{On} exists.

Proof: the proof of this theorem is simple and straight forward.

The potential drop across $Y_1 = (V_{1o})^1 = (V_{1o})^1 + (V_{oo})^1 = (V_{oo})^1 - V_{o1}$

Current, $Y_1 = Y_1 (V_{1o})^1 = Y_1 ((V_{oo})^1 - V_{o1})$

Similarly current through $Y_2 = Y_2 (V_{2o})^1 = Y_2((V_{oo})^1 - V_{o2})$

Finally current through $Y_n = Y_n (V_{no})^1 = Y_n ((V_{oo})^1 - V_{on})$

Applying KCL at node $(O)^1$

$$(I_{10})^1 + (I_{20})^1 + \dots + (I_{n0})^1 = 0$$

$$((V_{oo})^1 - V_{o1}) Y_1 + ((V_{oo})^1 - V_{o2}) Y_2 + \dots + ((V_{oo})^1 - V_{on}) Y_n = 0$$

$$(V_{oo})^1 (Y_1 + Y_2 + \dots + Y_n) = V_{o1} Y_1 + V_{o2} Y_2 + \dots + V_{on} Y_n$$

$$(V_{oo})^1 = \frac{V_{o1} Y_1 + V_{o2} Y_2 + \dots + V_{on} Y_n}{(Y_1 + Y_2 + \dots + Y_n)}$$

$$(V_{oo})^1 = \frac{\sum_{k=1}^n V_{ok} Y_k}{\sum_{k=1}^n Y_k}$$

In this theorem, voltage drop is taken as positive.

And also this method is very useful in solving 3-phase unbalanced star connected load using neutral displacement method.