
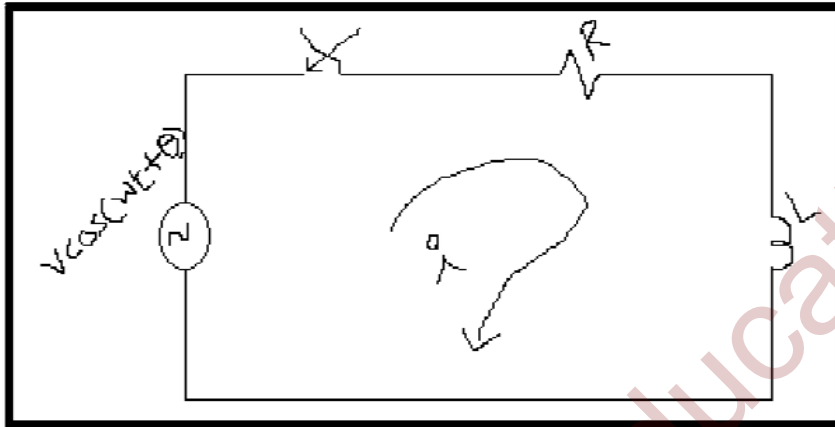


AC Transients

Sinusoidal Response of R-L Circuit:

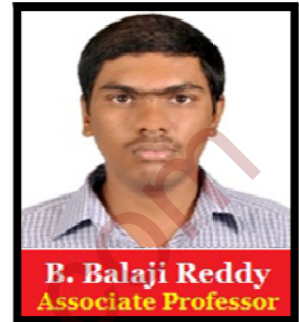Consider a circuit consisting of resistance and inductance are connected as shown in fig. the switch S is closed at $t=0$. At $t=0$, sinusoidal voltage $V\cos(\omega t + \theta)$ applied to RL circuit, where V is the amplitude of the wave and θ is the phase angle. Application of Kirchoff's laws we can determine the differential equations.



$$V\cos(\omega t + \theta) = iR + L \frac{di}{dt} \text{ ----- (1)}$$

$$\frac{di}{dt} + \frac{R}{L} i = \frac{V}{L} \cos(\omega t + \theta) \text{ ----- (2)}$$

The corresponding characteristic equation is

$$(D + \frac{R}{L}) i = \frac{V}{L} \cos(\omega t + \theta) \text{ ----- (3)}$$

For the above equation, the solution consists of two parts. One is complementary function and other is particular integral.

The complementary function of the solution is

$$i_c = c e^{-t(\frac{R}{L})} \text{ ----- (4)}$$

The particular solution can be obtained by using undetermined co-efficient.

By assuming,

$$i_p = A \cos(\omega t + \theta) + B \sin(\omega t + \theta) \text{ ----- (5)}$$

$$i_p^1 = -Aw \sin(\omega t + \theta) + Bw \cos(\omega t + \theta) \text{ ----- (6)}$$

Substituting equations 5 & 6 in 3 we get,

$$\{-Aw \sin(\omega t + \theta) + B\omega \cos(\omega t + \theta) + \frac{R}{L}[A \cos(\omega t + \theta) + B \sin(\omega t + \theta)]\} = \frac{V}{L} \cos(\omega t + \theta)$$

$$(-A\omega + \frac{BR}{L})\sin(\omega t + \theta) + (B\omega + \frac{AR}{L})\cos(\omega t + \theta) = \frac{V}{L} \cos(\omega t + \theta)$$

Comparing cosine terms and sine terms, we get

$$-A\omega + \frac{BR}{L} = 0$$

$$B\omega + \frac{AR}{L} = \frac{V}{L}$$

From the above equations we have

$$A = V \frac{R}{R^2 + (\omega L)^2}$$

$$B = V \frac{\omega L}{R^2 + (\omega L)^2}$$

Substituting the A and B values in equation (5) we get

$$i_p = V \frac{R}{R^2 + (\omega L)^2} \cos(\omega t + \theta) + V \frac{\omega L}{R^2 + (\omega L)^2} \sin(\omega t + \theta) \text{ ----- (7)}$$

Putting $M \cos \phi = V \frac{R}{R^2 + (\omega L)^2}$

$$M \sin \phi = V \frac{\omega L}{R^2 + (\omega L)^2}$$

To find M and ϕ , we divide one equation by the other

$$\tan \phi = \frac{\sin \phi}{\cos \phi} = \frac{\omega L}{R}$$

Squaring both equations and adding, we get

$$M^2 \cos^2 \phi + M^2 \sin^2 \phi = V \frac{V}{R^2 + (\omega L)^2}$$

$$M = \frac{V}{\sqrt{R^2 + (\omega L)^2}}$$

The particular current becomes

$$i_p = \frac{V}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t + \theta - \tan^{-1} \frac{\omega L}{R}) \text{ ----- (8)}$$

The complete solution for the current, $i = i_c + i_p$

$$i = c e^{-t(\frac{R}{L})} + \frac{V}{\sqrt{R^2+(wL)^2}} \cos(wt + \theta - \tan^{-1} \frac{wL}{R})$$


Since the inductor does not allow sudden changes in currents, at $t=0$, $i=0$

$$c = \frac{-V}{\sqrt{R^2+(wL)^2}} \cos(\theta - \tan^{-1} \frac{wL}{R})$$

The complete solution for the current is,

$$i = e^{-t(\frac{R}{L})} \left[\frac{-V}{\sqrt{R^2+(wL)^2}} \cos(\theta - \tan^{-1} \frac{wL}{R}) \right] + \frac{V}{\sqrt{R^2+(wL)^2}} \cos(wt + \theta - \tan^{-1} \frac{wL}{R})$$

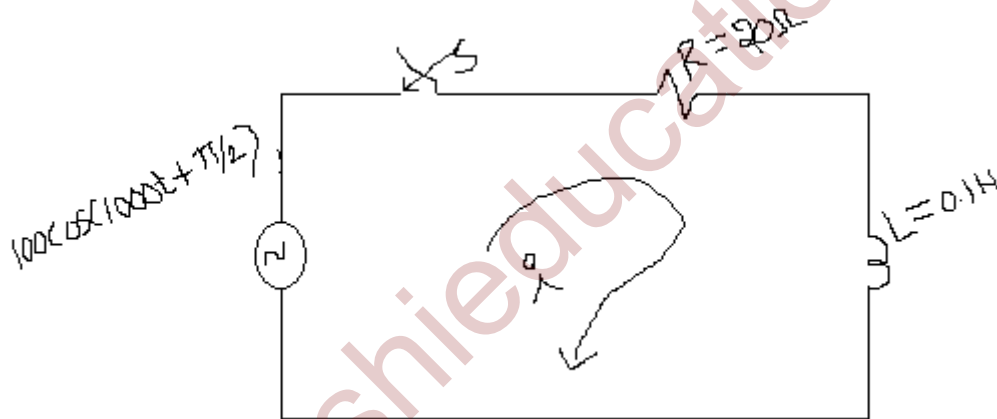Example: In the circuit shown in fig. determine the complete solution for the current, when the switch S is closed at $t=0$. Applied voltage is $V(t) = 1000\cos(1000t + \frac{\pi}{2})$, Resistance= 20Ω , and inductance= $0.1H$.



$$1000 \cos(1000t + \frac{\pi}{2}) = 20i + 0.1 \frac{di}{dt}$$

$$\frac{di}{dt} + 200 i = 1000 \cos(1000t + \frac{\pi}{2})$$

The corresponding characteristic equation is

$$(D + 200) i = 1000 \cos(1000t + \frac{\pi}{2})$$

The complementary function of the solution is

$$i_c = c e^{-t(\frac{R}{L})} = c e^{-200t}$$

The particular current becomes

$$i_p = \frac{1000}{\sqrt{20^2+(1000*0.1)^2}} \cos(1000t + \frac{\pi}{2} - \tan^{-1} \frac{1000}{20})$$

$$i_p = 0.98 \cos(1000t + \frac{\pi}{2} - 78.6^\circ)$$

The complete solution for the current, $i = i_c + i_p$

$$i = c e^{-200t} + 0.98 \cos(1000t + \frac{\pi}{2} - 78.6^\circ)$$


At $t=0$, the current flowing through the circuit is zero, $i = 0$

$$c = -0.98 \cos(\frac{\pi}{2} - 78.6^\circ)$$

The complete solution for the current, $i = i_c + i_p$

$$i = [-0.98 \cos(\frac{\pi}{2} - 78.6^\circ)] e^{-200t} + 0.98 \cos(1000t + \frac{\pi}{2} - 78.6^\circ)$$

Sinusoidal Response of R-C Circuit:

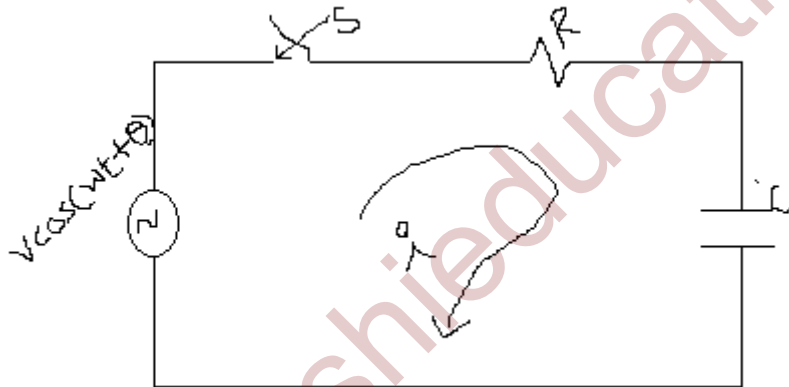

Consider a circuit consisting of resistance and capacitance in series as shown in fig. the switch S is closed at $t=0$. At $t=0$, sinusoidal voltage $V \cos(wt + \theta)$ applied to RL circuit, where V is the amplitude of the wave and θ is the phase angle. Application of Kirchoff's laws we can determine the differential equations.

$$V \cos(wt + \theta) = Ri + \frac{1}{C} \int i dt \text{ ----- (1)}$$

$$-Vw \sin(wt + \theta) = R \frac{di}{dt} + \frac{i}{C} \text{ ----- (2)}$$

$$(D + \frac{1}{RC}) i = \frac{-Vw}{R} \sin(wt + \theta) \text{ ----- (3)}$$

The complementary function, $i_c = c e^{\frac{-t}{RC}}$

The particular solution can be obtained by using undetermined coefficients.

$$i_p = A \cos(\omega t + \theta) + B \sin(\omega t + \theta) \text{ ----- (4)}$$

$$i_p^1 = -A\omega \sin(\omega t + \theta) + B\omega \cos(\omega t + \theta) \text{ ----- (5)}$$

Substituting equation 4 & 5 in 3 we get

$$\{-A\omega \sin(\omega t + \theta) + B\omega \cos(\omega t + \theta)\} +$$

$$\frac{1}{RC} \{ A \cos(\omega t + \theta) + B \sin(\omega t + \theta) \} = \frac{-V\omega}{R} \sin(\omega t + \theta)$$

Comparing both sides,

$$-A\omega + \frac{B}{RC} = \frac{-V\omega}{R}$$

$$B\omega + \frac{A}{RC} = 0$$

So we get,

$$A = \frac{VR}{R^2 + (\frac{1}{\omega C})^2}$$

$$B = \frac{-V}{\omega C [R^2 + (\frac{1}{\omega C})^2]}$$

Substituting A and B values in 4 we get

$$i_p = \frac{VR}{R^2 + (\frac{1}{\omega C})^2} \cos(\omega t + \theta) - \frac{V}{\omega C [R^2 + (\frac{1}{\omega C})^2]} \sin(\omega t + \theta)$$

Putting $M \cos \phi = \frac{VR}{R^2 + (\frac{1}{\omega C})^2}$

$$M \sin \phi = \frac{V}{\omega C [R^2 + (\frac{1}{\omega C})^2]}$$

To find M and ϕ , we divide one equation by the other

$$\tan \phi = \frac{\sin \phi}{\cos \phi} = \frac{1}{\omega CR}$$

Squaring both equations and adding, we get

$$M^2 \cos^2 \phi + M^2 \sin^2 \phi = V^2 \frac{1}{R^2 + (\frac{1}{\omega C})^2}$$

$$M = \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C})^2}}$$

The particular current becomes

$$i_p = \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \cos(\omega t + \theta + \tan^{-1} \frac{1}{\omega CR}) \text{ ----- (8)}$$

The complete solution for the current, $i = i_c + i_p$

$$i = c e^{-t(\frac{1}{RC})} + \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \cos(\omega t + \theta + \tan^{-1} \frac{1}{\omega CR})$$

Since the capacitor does not allow sudden changes in voltages, at $t=0$, $i = \frac{V}{R} \cos \theta$


$$\frac{V}{R} \cos \theta = c + \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \cos(\theta + \tan^{-1} \frac{1}{\omega CR})$$

Therefore, $c = \frac{V}{R} \cos \theta - \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \cos(\theta + \tan^{-1} \frac{1}{\omega CR})$

The complete solution for the current is,

$$i = e^{-t(\frac{1}{RC})} [\frac{V}{R} \cos \theta - \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \cos(\theta + \tan^{-1} \frac{1}{\omega CR})] + \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \cos(\omega t + \theta + \tan^{-1} \frac{1}{\omega CR})$$

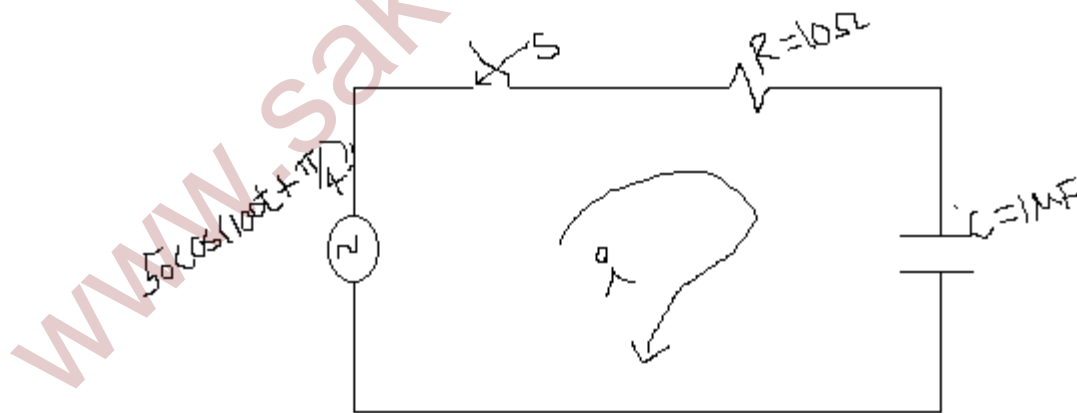Example: In the circuit shown in fig. determine the complete solution for the current, when the switch S is closed at $t=0$. Applied voltage is $V(t) = 50\cos(100t + \frac{\pi}{4})$, Resistance= 10Ω , and capacitance= $1\mu F$.



$$50\cos(100t + \frac{\pi}{4}) = 10i + \frac{1}{1 \cdot 10^{-6}} \int i dt$$

$$- 500\sin(100t + \frac{\pi}{4}) = 10\frac{di}{dt} + \frac{i}{1 \cdot 10^{-6}}$$

$$(D + \frac{1}{1 \times 10^{-5}}) i = -500 \sin(100t + \frac{\pi}{4})$$

The complementary function, $i_c = c e^{\frac{-t}{RC}} = c e^{\frac{-t}{10^{-5}}}$

The particular current becomes

$$i_p = \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \cos(\omega t + \theta + \tan^{-1} \frac{1}{\omega CR})$$

$$i_p = \frac{50}{\sqrt{10^2 + (\frac{1}{100 \times 10^{-6} \times 10})^2}} \cos(\omega t + \frac{\pi}{4} + \tan^{-1} \frac{1}{100 \times 10^{-6} \times 10})$$

$$= 4.99 \times 10^{-3} \cos(100t + \frac{\pi}{4} + 89.94^\circ)$$

At $t=0$, the current flowing through the circuit is,

$$\frac{V}{R} \cos \theta = \frac{50}{10} \cos \frac{\pi}{4} = 3.53 \text{ A}$$

The complete solution for the current, $i = i_c + i_p$

$$i = c e^{\frac{-t}{10^{-5}}} + 4.99 \times 10^{-3} \cos(100t + \frac{\pi}{4} + 89.94^\circ)$$

At $t=0$, $i=3.53 \text{ A}$ then we get c value


$$3.53 = c e^{\frac{-t}{10^{-5}}} + 4.99 \times 10^{-3} \cos(100t + \frac{\pi}{4} + 89.94^\circ)$$

$$c = [3.53 - 4.99 \times 10^{-3} \cos(100t + \frac{\pi}{4} + 89.94^\circ)]$$

The complete solution for the current,

$$i = [3.53 - 4.99 \times 10^{-3} \cos(100t + \frac{\pi}{4} + 89.94^\circ)] e^{\frac{-t}{10^{-5}}} + 4.99 \times 10^{-3} \cos(100t + \frac{\pi}{4} + 89.94^\circ)$$

Sinusoidal Response of R-L-C Circuit:

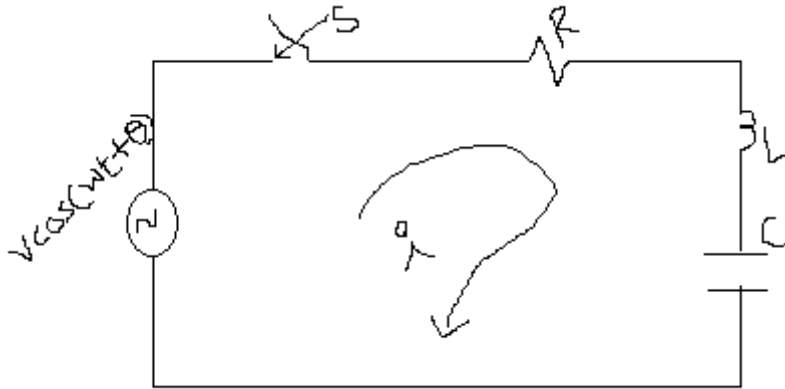

Consider a circuit consisting of resistance, inductance and capacitance in series as shown in fig. Switch s is closed at $t=0$. At $t=0$, a sinusoidal voltage $V\cos(\omega t + \theta)$ applied to RLC circuit, where V is the amplitude of the wave and θ is the phase angle. Application of Kirchoff's laws we can determine the differential equations.

$$V\cos(\omega t + \theta) = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt \text{ ----- (1)}$$

By differentiating above equation we get,

$$-V\omega\sin(\omega t + \theta) = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i \text{ ----- (2)}$$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = -V\omega\sin(\omega t + \theta) \text{ ----- (3)}$$

$$(D^2 + \frac{R}{L} D + \frac{1}{LC})i = -\frac{V\omega}{L} \sin(\omega t + \theta) \text{ ----- (4)}$$

The particular solution can be obtained by using undetermined coefficients.

$$i_p = A \cos(\omega t + \theta) + B \sin(\omega t + \theta) \text{ ----- (5)}$$

$$i_p^1 = -A\omega \sin(\omega t + \theta) + B\omega \cos(\omega t + \theta) \text{ ----- (6)}$$

$$i_p^{11} = -A\omega^2 \cos(\omega t + \theta) - B\omega^2 \sin(\omega t + \theta) \text{ ----- (7)}$$

Substituting 5,6 & 7 in equation 4 we get,

$$\begin{aligned} & \{-A\omega^2 \cos(\omega t + \theta) - B\omega^2 \sin(\omega t + \theta)\} + \frac{R}{L} \{-A\omega \sin(\omega t + \theta) + B\omega \cos(\omega t + \theta)\} \\ & + \frac{1}{LC} \{A \cos(\omega t + \theta) + B \sin(\omega t + \theta)\} = -\frac{V\omega}{L} \sin(\omega t + \theta) \end{aligned}$$

Comparing both the sides, sine and cosine coefficients we get,

$$-B\omega^2 - A \frac{\omega R}{L} + \frac{B}{LC} = -\frac{V\omega}{L}$$

$$A \left(\frac{\omega R}{L}\right) + B \left(\omega^2 - \frac{1}{LC}\right) = \frac{V\omega}{L} \text{----- (8)}$$

$$-A\omega^2 + B \frac{\omega R}{L} + \frac{A}{LC} = 0$$

$$A \left(\omega^2 - \frac{1}{LC}\right) - B \left(\frac{\omega R}{L}\right) = 0 \text{----- (9)}$$

Solving equations 8 & 9 we get

$$A = \frac{V * \frac{\omega^2 R}{L^2}}{\left[\left(\frac{\omega R}{L}\right)^2 - \left(\omega^2 - \frac{1}{LC}\right)^2\right]}$$

$$B = \frac{\left(\omega^2 - \frac{1}{LC}\right) * V\omega}{L\left[\left(\frac{\omega R}{L}\right)^2 - \left(\omega^2 - \frac{1}{LC}\right)^2\right]}$$

Substituting A and B values in 5 we get

$$i_p = \frac{V * \frac{\omega^2 R}{L^2}}{\left[\left(\frac{\omega R}{L}\right)^2 - \left(\omega^2 - \frac{1}{LC}\right)^2\right]} \cos(\omega t + \theta) + \frac{\left(\omega^2 - \frac{1}{LC}\right) * V\omega}{L\left[\left(\frac{\omega R}{L}\right)^2 - \left(\omega^2 - \frac{1}{LC}\right)^2\right]} \sin(\omega t + \theta) \text{---- (10)}$$

Putting $M \cos \phi = \frac{V * \frac{\omega^2 R}{L^2}}{\left[\left(\frac{\omega R}{L}\right)^2 - \left(\omega^2 - \frac{1}{LC}\right)^2\right]}$

$$M \sin \phi = \frac{\left(\omega^2 - \frac{1}{LC}\right) * V\omega}{L\left[\left(\frac{\omega R}{L}\right)^2 - \left(\omega^2 - \frac{1}{LC}\right)^2\right]}$$

To find M and ϕ , we divide one equation by the other

$$\tan \phi = \frac{\sin \phi}{\cos \phi} = \frac{\left(\omega L - \frac{1}{\omega C}\right)}{R}$$

Squaring both equations and adding, we get

$$M^2 \cos^2 \phi + M^2 \sin^2 \phi = V \frac{V}{R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2}$$

$$M = \frac{V}{\sqrt{R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2}}$$

The particular current becomes

$$i_p = \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C} - \omega L)^2}} \cos(\omega t + \theta + \tan^{-1} \frac{\frac{1}{\omega C} - \omega L}{R})$$

The complementary function is similar to that of DC series RLC circuit.

$$D^2 + \frac{R}{L} D + \frac{1}{LC} = 0$$

The roots above equation are,

$$D_1, D_2 = -\frac{R}{2L} \pm \sqrt{(\frac{R}{2L})^2 - \frac{1}{LC}}$$

By assuming, $K_1 = -\frac{R}{2L}$ and $K_2 = \sqrt{(\frac{R}{2L})^2 - \frac{1}{LC}}$

$$D_1 = K_1 + K_2$$

$$D_2 = K_1 - K_2$$

Here K_2 may be positive or negative or zero.

K_2 Is positive, when $(\frac{R}{2L})^2 > \frac{1}{LC}$

The roots are real and unequal, and give the over damped response as shown in fig. then equation (4) becomes

$$[D - (K_1 + K_2)][[D - (K_1 - K_2)]]i = 0$$

The solution for the above equation is,

$$i_c = c_1 e^{(K_1 + K_2)t} + c_2 e^{(K_1 - K_2)t}$$

Therefore the complete solution is, $i = i_c + i_p$

$$i = c_1 e^{(K_1 + K_2)t} + c_2 e^{(K_1 - K_2)t} + \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C} - \omega L)^2}} \cos(\omega t + \theta + \tan^{-1} \frac{\frac{1}{\omega C} - \omega L}{R})$$

K_2 Is negative, when $(\frac{R}{2L})^2 < \frac{1}{LC}$. The roots are complex conjugate, and give the under damped the equation as shown in becomes

$$[D - (K_1 + jK_2)][[D - (K_1 - jK_2)]]i = 0$$

The solution for above equation is,

$$i_c = e^{K_1 t} [c_1 \cos K_2 t + c_2 \sin K_2 t]$$

Therefore the complete solution is, $i = i_c + i_p$

$$i = e^{K_1 t} [c_1 \cos K_2 t + c_2 \sin K_2 t] + \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C} - \omega L)^2}} \cos(\omega t + \theta + \tan^{-1} \frac{\frac{1}{\omega C} - \omega L}{R})$$

K_2 Is zero, when $(\frac{R}{2L})^2 = \frac{1}{LC}$. The roots are equal, and give the critically damped response as shown in fig. the equation becomes

$$[D - K_1][[D - K_2]]i=0$$


The solution for above equation is

$$i_c = e^{K_1 t} [c_1 + c_2 t]$$

Therefore the complete solution is, $i = i_c + i_p$

$$i = e^{K_1 t} [c_1 + c_2 t] + \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C} - \omega L)^2}} \cos(\omega t + \theta + \tan^{-1} \frac{\frac{1}{\omega C} - \omega L}{R})$$

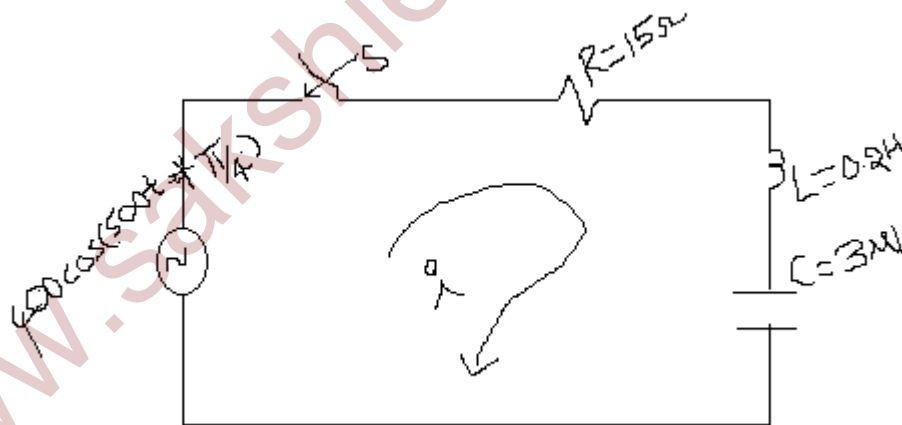Example: In the circuit shown in fig. determine the complete solution for the current, when the switch S is closed at $t=0$. Applied voltage is $V(t) = 400 \cos(500t + \frac{\pi}{4})$, Resistance= 15Ω , inductance= $0.2H$ and capacitance= $3\mu F$.



By applying Kirchoff's voltage law to the circuit,

$$400 \cos(500t + \frac{\pi}{4}) = 15 i(t) + 0.2 \frac{di}{dt} + \frac{1}{3 \times 10^{-6}} \int i(t) dt$$

By differentiating above equation we get,

$$-2 \times 10^5 \sin(500t + \frac{\pi}{4}) = 15 \frac{di}{dt} + 0.2 \frac{d^2 i}{dt^2} + \frac{1}{3 \times 10^{-6}} i$$

$$(D^2 + 75 D + 16.7 * 10^5)i = - 10 * 10^5 \sin(500t + \frac{\pi}{4})$$

The roots of the characteristic equation are,

$$D_1 = -37.5 + j1290 \text{ and } D_2 = -37.5 - j1290$$

$$[D - (K_1 + jK_2)][D - (K_1 - jK_2)]i = 0$$

The solution for above equation is,

$$i_c = e^{-37.5t} [c_1 \cos 1290t + c_2 \sin 1290t]$$

The particular solution is

$$i_p = \frac{V}{\sqrt{R^2 + (\frac{1}{\omega C} - \omega L)^2}} \cos(\omega t + \theta + \tan^{-1} \frac{\frac{1}{\omega C} - \omega L}{R})$$

$$i_p = 0.71 \cos(500t + \frac{\pi}{4} + 88.5^\circ)$$

Therefore the complete solution is, $i = i_c + i_p$

$$i = e^{-37.5t} [c_1 \cos 1290t + c_2 \sin 1290t] + 0.71 \cos(500t + \frac{\pi}{4} + 88.5^\circ)$$

At $t=0$, $i_0 = 0$

$$c_1 = 0.71 \cos(\frac{\pi}{4} + 88.5^\circ) = 0.49$$

Differentiating the current equation, we get

$$\frac{di}{dt} = e^{-37.5t} [-1290c_1 \sin 1290t + 1290c_2 \cos 1290t] - 37.5e^{-37.5t} [c_1 \cos 1290t + c_2 \sin 1290t] - 500 * 0.71 \sin(500t + \frac{\pi}{4} + 88.5^\circ)$$

At $t=0$, $\frac{di}{dt} = 1414$

$$1414 = e^{-37.5t} [-1290c_1 \sin 1290t + 1290c_2 \cos 1290t] - 37.5e^{-37.5t} [c_1 \cos 1290t + c_2 \sin 1290t] - 500 * 0.71 \sin(500t + \frac{\pi}{4} + 88.5^\circ)$$

Solving this we get, $c_2 = 1.31$

Therefore the complete solution is,

$$i = e^{-37.5t} [0.49 \cos 1290t + 1.31 \sin 1290t] + 0.71 \cos(500t + 133.5^\circ)$$